

Template Week 2 – Logic

Student number:

577534

Assignment 2.1: Parking lot

Which gates do you need?

AND gate

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android or iPhone

Which gates do you need?

XOR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table


A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

How can the design be simplified?

Use **two NAND gates** to create an AND gate.


Assignment 2.4: Getting to know Logisim evolution

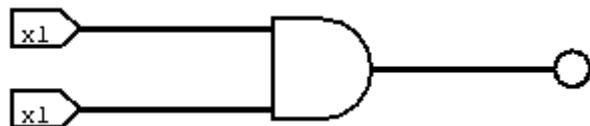Screenshot of the design with your name and student number in it:




Ebrahim Amin

577534

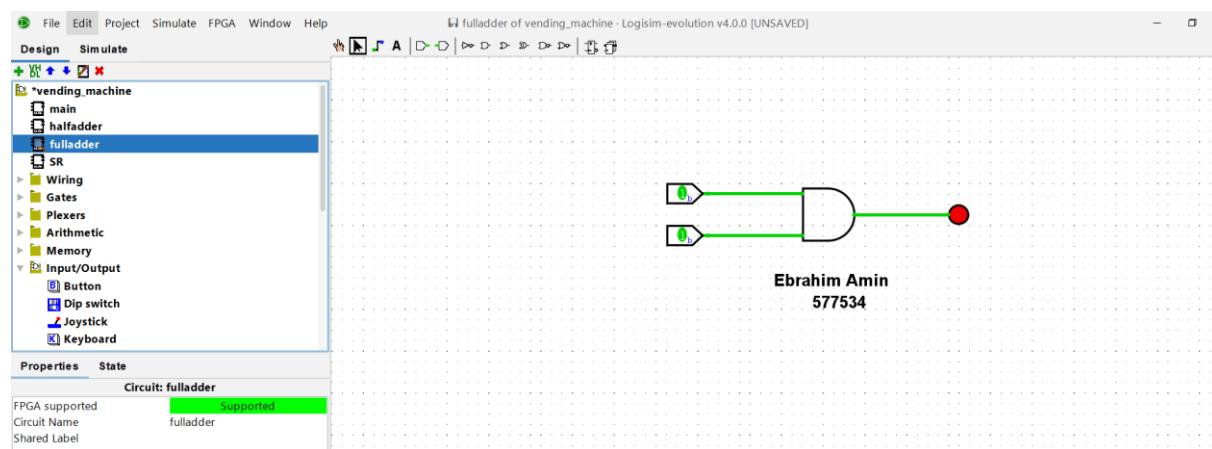


Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

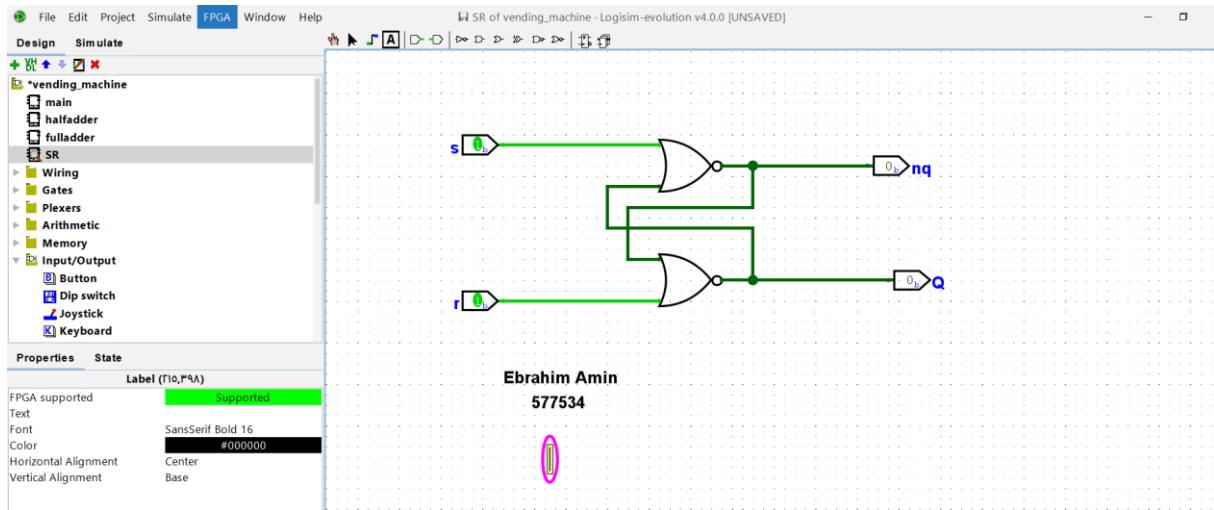

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

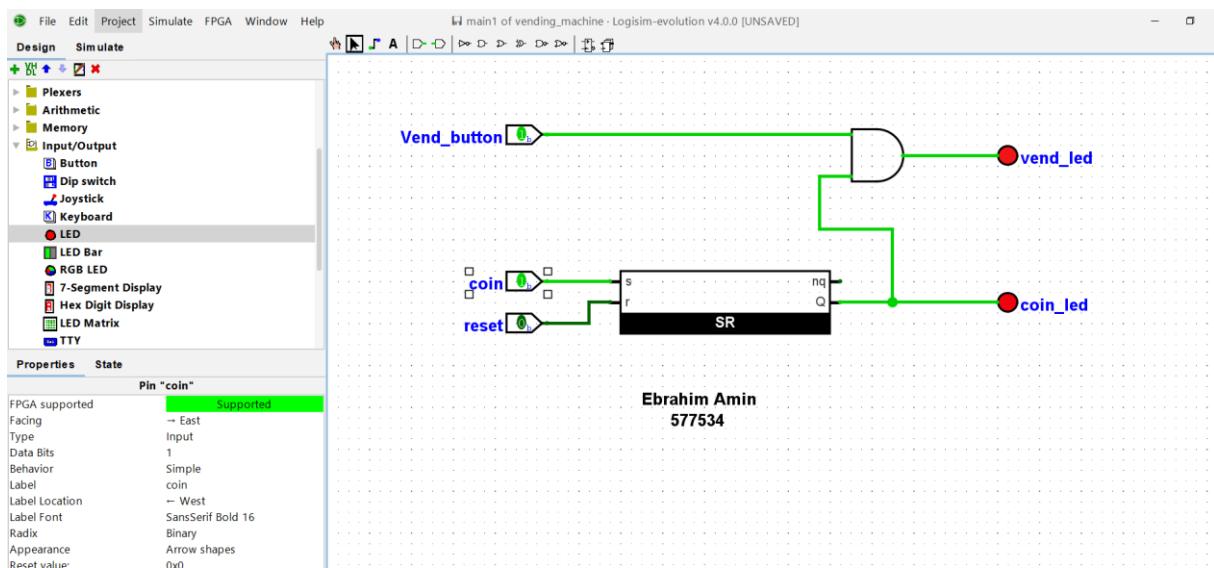

Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

1-bitwise & AND operator.

```
public class Main {  
    public static void main(String[] args) {  
        int number = 5;  
        if ((number & 1) == 1)  
            System.out.println("number is odd");  
        else  
            System.out.println("number is even");  
    }  
}
```

2

```
public class Main {  
    public static void main(String[] args) {  
        int number = 4;  
        if ((number & (number - 1)) == 0)  
            System.out.println("number is a power of 2");  
        else  
            System.out.println("number isn't a power of 2");  
    }  
}
```

3

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;
```

```

int userPermissions = 7;

if ((userPermissions & READ) != 0)
    System.out.println("User has read permissions");

else
    System.out.println("User can't read. No permissions.");

}
}

```

4-bitwise | OR operator

```

public class Main {

    public static void main(String[] args) {

        final int READ = 4;
        final int WRITE = 2;
        final int EXECUTE = 1;

        int userPermissions = 0;

        // Add READ and EXECUTE permissions
        userPermissions = READ | EXECUTE;

        System.out.println("User permissions: " + userPermissions);

    }
}

```

5- bitwise ^ XOR operator

```

public class Main {

    public static void main(String[] args) {

        final int READ = 4;
        final int WRITE = 2;
        final int EXECUTE = 1;

```

```

int userPermissions = 6; // currently READ + WRITE (110)

// Remove WRITE so only READ remains
userPermissions = userPermissions ^ WRITE;

System.out.println("User permissions: " + userPermissions);

}

}

```

6 bitwise ~ NOT operator.

```

public class Main {

    public static void main(String[] args) {

        int number = 5;

        // apply two's complement
        number = ~number + 1;

        System.out.println("Number: " + number);
    }
}

```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```
public class Main {  
  
    public static void main(String[] args) {  
        int number = 5;  
        int choice = 1;  
  
        switch (choice) {  
            case 1:  
                isOdd(number);  
                break;  
            case 2:  
                isPowerOfTwo(number);  
                break;  
            case 3:  
                twoComplement(number);  
                break;  
        }  
    }  
  
    public static void isOdd(int number) {  
        if ((number & 1) == 1)  
            System.out.println("The number is odd.");  
        else  
            System.out.println("The number is even.");  
    }  
  
    public static void isPowerOfTwo(int number) {  
        if (number > 0 && (number & (number - 1)) == 0)  
    }  
}
```

```

        System.out.println("The number is a power of 2.");
    else
        System.out.println("The number is NOT a power of 2.");
    }

public static void twosComplement(int number) {
    int result = ~number + 1;
    System.out.println("Two's complement: " + result);
}

```

The number is odd.

```

public class Main {
    public static void main(String[] args) {
        int number = 5;
        int choice = 1;

        switch (choice) {
            case 1:
                isOdd(number);
                break;
            case 2:
                isPowerOfTwo(number);
                break;
            case 3:
                twosComplement(number);
                break;
        }
    }

    public static void isOdd(int number) {
        if ((number & 1) == 1)
            System.out.println("The number is odd.");
        else
            System.out.println("The number is even.");
    }

    public static void isPowerOfTwo(int number) {
        if (number > 0 && (number & (number - 1)) == 0)
            System.out.println("The number is a power of 2.");
        else
            System.out.println("The number is NOT a power of 2.");
    }

    public static void twosComplement(int number) {
        int result = ~number + 1;
        System.out.println("Two's complement: " + result);
    }
}

```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)